

Series $Z = R + j\omega L + 1/j\omega C$



At f_0 : $X_L = X_C$, $\text{Im}(Z) = 0$

$Z_{\text{min}} = R$ (purely resistive)

Parallel $Z \rightarrow \text{max at } f_0$

