

Series  $Z = R + j\omega L + 1/j\omega C$



At  $f_0$ :  $X_L = X_C$ ,  $\text{Im}(Z) = 0$   
 $Z_{\text{min}} = R$  (purely resistive)

Parallel  $Z \rightarrow \text{max at } f_0$

